

ELEN0037

Microelectronics

Tutorials

Pouyan Ebrahimbabaie, Vinayak Pachkawade, Thomas Schmitz

With special thanks to Vincent Pierlot

University of Liège - Montefiore Institute
EMMI Unit: Electronics, Microsystems, Measurements, and Instrumentation

Tutorial 5: Filters (BiQuad, Gm-C, MOSFET-C, etc)

Biquad filters (summary)

General form $H(s) = \frac{k_2 s^2 + k_1 s + k_0}{s^2 + (\Omega_0/Q) s + \Omega_0^2}$

Low Pass $H(s) = \frac{\Omega_0^2}{s^2 + (\Omega_0/Q) s + \Omega_0^2}$

Band Pass $H(s) = \frac{(\Omega_0/Q) s}{s^2 + (\Omega_0/Q) s + \Omega_0^2}$

Band Stop $H(s) = \frac{s^2 + \Omega_0^2}{s^2 + (\Omega_0/Q) s + \Omega_0^2}$

High Pass $H(s) = \frac{s^2}{s^2 + (\Omega_0/Q) s + \Omega_0^2}$

Exercise 1 (1st, P10.10/2nd, P14.18)

Using the bilinear transform, design a bandpass filter with a $Q = 20$ (in the continuous-time domain) and a peak gain of 1 at $f_0 = f_s/100$.¹ The (continuous) transfer function of the biquad bandpass filter is given by:


$$H(s) = \frac{k_1 s}{s^2 + (\Omega_0/Q) s + \Omega_0^2}.$$

$${}^1 H(s) = \frac{0.00157s}{s^2 + 0.00157s + 0.0009876},$$

$$H(z) = \frac{0.00157z^2 - 0.00157}{1.0026z^2 - 1.998z + 0.99942}$$

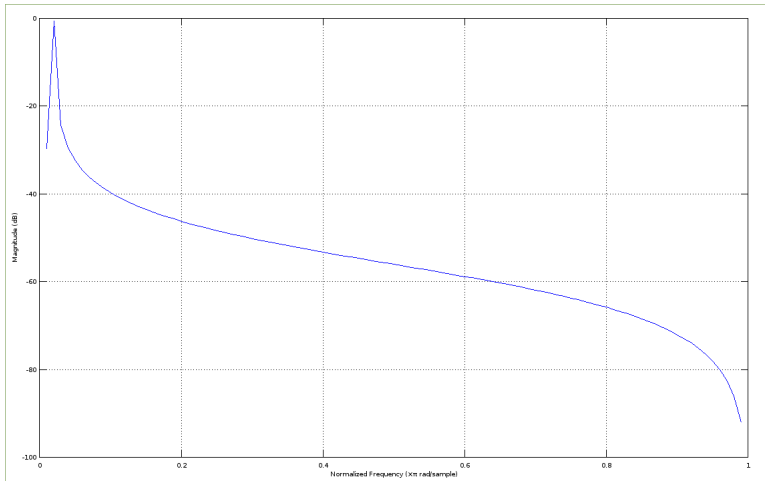Exercise 1 (frequency response)

```
freqz([0.00157 0 -0.00157],[1.0026 -1.998 0.99942],100)
```




Peak gain = 0dB = 1.

Peak gain @ 0.02 of $f_s/2$, \Rightarrow peak gain @ $f_0 = f_s/100$.

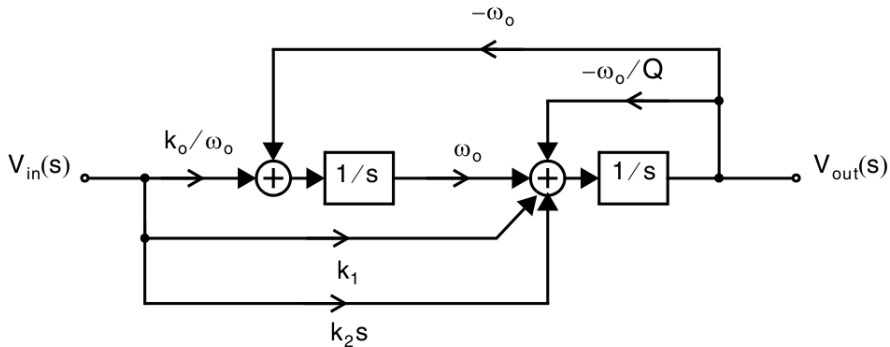Exercise 2 (2nd, P12.1)


Find all of the signal path gains that are required in the general second-order (biquad) continuous-time filter to realize a bandpass filter with a center frequency of $\omega_0 = 2\pi \times 34 \text{ MHz}$, a Q-factor of 3, and a peak gain of 1.²



$$^2 Q = 3, \omega_0 = 213.63 \cdot 10^6 \text{ Hz}, k_1 = 71.21 \cdot 10^6$$

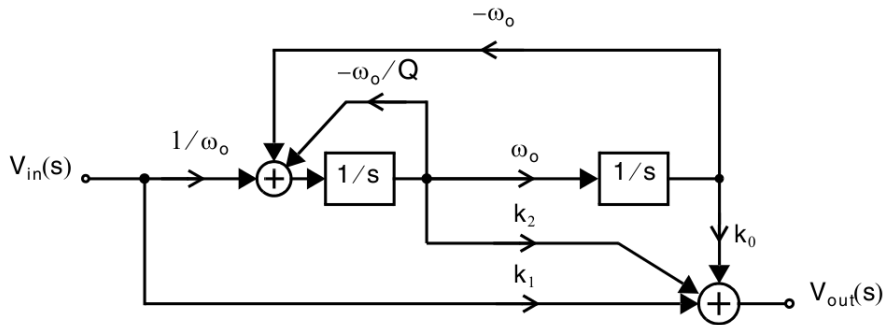Exercise 3 (2nd, P12.2)


Find the transfer function of the general biquad signal flow graph represented hereafter.³



$$^3 H(s) = \left[k_1 s^2 + \left(k_1 \frac{\omega_0}{Q} + \frac{k_2}{\omega_0} \right) s + (k_1 \omega_0^2 + k_0) \right] / [s^2 + (\omega_0/Q)s + \omega_0^2]$$

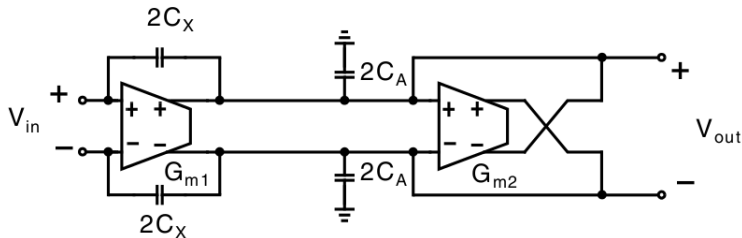Exercise 4 (1st, P15.2)

Based on the block diagram represented hereafter, find the transconductance values for a first-order filter with a DC gain of 10, a cutoff frequency of 15 MHz , and no finite zero. Assume the integrating capacitors are sized $C_A = 5\text{ pF}$.⁴




The transfer function is given by:

$$H(s) = \frac{\left(\frac{C_X}{C_A + C_X}\right) s + \left(\frac{G_{m1}}{C_A + C_X}\right)}{s + \left(\frac{G_{m2}}{C_A + C_X}\right)}$$

⁴ $C_X = 0$, $G_{m1} = 4.71\text{ mA/V}$, $G_{m2} = 0.47\text{ mA/V}$

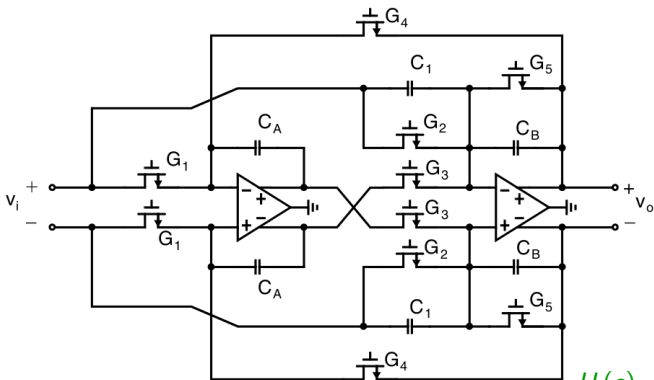Exercise 5 (1st, P15.16)

Using two-transistors integrators, design a MOSFET-C second-order low-pass filter with a cutoff frequency of 1 MHz , $Q = 1$, and a DC gain of 2. Let $C_A = C_B = 10\text{ pF}$, $V_C = 3\text{ V}$, and $V_X = 0\text{ V}$.⁵⁶



$$H(s) = -\frac{\left(\frac{C_1}{C_B}\right)s^2 + \left(\frac{G_2}{C_B}\right)s + \left(\frac{G_1 G_3}{C_A C_B}\right)}{s^2 + \left(\frac{G_5}{C_B}\right)s + \left(\frac{G_3 G_4}{C_A C_B}\right)}$$

⁵ $C_1 = G_2 = 0$, $G_5 = 63\ \mu\text{A/V}$, $G_3 G_4 = 3.95 \cdot 10^{-9}$, $G_1 G_3 = 7.9 \cdot 10^{-9}$

⁶ let $G_3 = 100\ \mu\text{A/V}$, $\frac{W_1}{L_1} = 0.39$, $\frac{W_3}{L_3} = 0.49$, $\frac{W_4}{L_4} = 0.2$, $\frac{W_5}{L_5} = 0.31$