

ELEN0037

Microelectronics

Tutorials

Pouyan Ebrahimbabaie, Vinayak Pachkawade, Thomas Schmitz

With special thanks to Vincent Pierlot

University of Liège - Montefiore Institute
EMMI Unit: Electronics, Microsystems, Measurements, and Instrumentation

Tutorial 7: Nyquist rate and oversampling A/D Converters

Signal to Quantization Noise Ratio (summary)


converter type	$SQNR_{max}$
Nyquist rate	$6.02N + 1.76$
Oversampling with no noise shaping	$6.02N + 1.76 + 10 \log OSR$
Oversampling with 1 st -order noise shaping	$6.02N + 1.76 - 5.17 + 30 \log OSR$
Oversampling with 2 nd -order noise shaping	$6.02N + 1.76 - 12.9 + 50 \log OSR$

$$OSR = \frac{f_s}{2f_0}$$

Note that these formulae are valid for an input sine wave (otherwise remove the $+1.76$ term), when the input signal spans the full range of the converter.

 Exercise 1 (1st, P13.1/2nd, P17.1)


What is the worst-case conversion time for an 18-bit dual-slope integrating A/D converter when the clock frequency is **5 MHz**?¹



$${}^1 T_{conv,max} = (2.2^N + 1) T_{clk} = 105 \text{ ms}$$

 Exercise 2 (1st, P13.2/2nd, P17.2)

Consider an 18-bit dual-slope integrating A/D converter, where V_{ref} equals 10 V , $C_1 = 100\text{ pF}$, and a clock frequency of 1 MHz is used. What value of R_1 should be chosen such that the opamp output never exceeds 10 V when $0\text{ V} < V_{in} < 10\text{ V}$?²



$$^2 R_1 > 2.62\text{ G}\Omega$$

Exercise 3 (1st, P13.5,6/2nd, P17.5,6)

What input-signal frequencies are completely attenuated by a 16-bit dual-slope integrating A/D converter, having a clock frequency of 1 MHz ?³ For this same converter, what is the attenuation of an input signal at 60 Hz ?⁴ Repeat the same, when $f_s = 100\text{ kHz}$.⁵

³all frequencies multiple of $1/T_1 = 1/2^N T_{clk} = 15.26\text{ Hz}$

⁴ $A_{f=60\text{ Hz}} = 1.98 \cdot 10^{-2} = -34\text{ dB}$

⁵all frequencies multiple of 1.53 Hz , $A_{f=60\text{ Hz}} = 5.09 \cdot 10^{-3} = -46\text{ dB}$

Exercise 4 (1st, P14.1)

Assuming oversampling with no noise shaping, find the approximate sampling rate required in order to obtain a maximum SQNR of 80 dB on a signal with a 1 kHz bandwidth using a 1-bit quantizer.⁶ Repeat the same problem, assuming a first-order modulator is used.⁷ Repeat the same problem, assuming a second-order modulator is used.⁸


⁶ $OSR = 16672472$, $f_s = 33.35\text{ GHz}$

⁷ $OSR = 380$, $f_s = 760\text{ kHz}$

⁸ $OSR = 50.4$, $f_s = 100.8\text{ kHz}$

 Exercise 5 (1st, P14.2,3,4/2nd, P18.4,5,6)

Find the output and state values of a 1st-order $\Sigma\Delta$ modulator using a 1-bit quantizer (± 1 output levels, *threshold* = 0), when a dc input $u(n) = 0.4$ is applied, and assuming the initial state $x(0) = 0.1$.⁹ At what frequency would a tone appear (relative to f_s)?¹⁰



The state equations of the first-order $\Sigma\Delta$ modulator are given by:

$$\begin{aligned}y(n) &= Q(x(n)) \\e(n) &= y(n) - x(n) \\x(n+1) &= x(n) + u(n) - y(n)\end{aligned}$$

⁹see next slide

¹⁰ $f_s/10$

Exercise 5 (continued)

The output and state values are given in the following table. Also, compute $e_{rms} = \Delta/\sqrt{12}$, $\sqrt{E\{e^2(n)\}}$, and $E\{y(n)\}$.¹¹

n	$u(n)$	$x(n)$	$y(n)$	$e(n)$	$x(n+1)$
0	0.4	0.1	1	0.9	-0.5
1	0.4	-0.5	-1	-0.5	0.9
2	0.4	0.9	1	0.1	0.3
3	0.4	0.3	1	0.7	-0.3
4	0.4	-0.3	-1	-0.7	1.1
5	0.4	1.1	1	-0.1	0.5
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots
10	0.4	0.1	1	0.9	-0.5

¹¹ $e_{rms} = 0.577 V$, $\sqrt{E\{e^2(n)\}} = 0.611 V$, $E\{y(n)\} = 0.4 V$

Exercise 5 (continued)

Repeat the same problem, with a dc input $u(n) = 1.1$, and the same initial state, to see if the internal state $x(n)$ of the modulator saturates.¹²

n	$u(n)$	$x(n)$	$y(n)$	$e(n)$	$x(n+1)$
0	1.1	0.1	1	0.9	0.2
1	1.1	0.2	1	0.8	0.3
2	1.1	0.3	1	0.7	0.4
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots

¹² $x(n)$ increases by 0.1 at each clock cycle, until saturation occurs

Exercise 5 (continued)

Repeat the same problem, with the following input sequence: $\{10, -10, 10, -10, 10, \dots\}$, and the same initial state, to see if the internal state $x(n)$ of the modulator saturates.

n	$u(n)$	$x(n)$	$y(n)$	$e(n)$	$x(n+1)$
0	10	0.1	1	0.9	9.1
1	-10	9.1	1	-8.1	-1.9
2	10	-1.9	-1	0.9	9.1
3	-10	9.1	1	-8.1	-1.9
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots

Exercise 6 (1st, P14.5,6/2nd, P18.3,7)

Given that an 8-bit A/D converter has a SQNR of 50 dB but is linear to 12 bits, what is the sampling rate required to achieve 12 bits of accuracy using straight oversampling on a signal bandwidth of 1 MHz ?¹³ What becomes the sampling rate if this 8-bit A/D converter is placed inside a first-order $\Sigma\Delta$ modulator?¹⁴ What becomes the sampling rate if the 8-bit A/D converter is placed inside a second-order $\Sigma\Delta$ modulator?¹⁵

¹³ $OSR = 256, f_s = 512 \text{ MHz}$

¹⁴ $OSR = 9.44, f_s = 18.88 \text{ MHz}$

¹⁵ $OSR = 5.49, f_s = 10.98 \text{ MHz}$