

ELEN0037

Microelectronics

Tutorials

Pouyan Ebrahimbabaie, Vinayak Pachkawade, Thomas Schmitz

With special thanks to Vincent Pierlot

University of Liège - Montefiore Institute
EMMI Unit: Electronics, Microsystems, Measurements, and Instrumentation

Tutorial 8: Noise Analysis and Modeling

Exercise 1 (1st, P4.2/2nd, P9.5)

Consider the sum of two noise sources of values -20 dBm and -23 dBm . Find the total noise power in dBm for the cases in which the two noise sources are (a) uncorrelated,¹ (b) $C = 0.3$,² (c) $C = +1$,³ and (d) $C = -1$.⁴ Use the following formula:

$$V_n^2 = V_{n1}^2 + V_{n2}^2 + 2CV_{n1}V_{n2},$$

or

$$P_n = P_{n1} + P_{n2} + 2C\sqrt{(P_1P_2)},$$

¹(a) $P_n = -18.24 \text{ dBm}$

²(b) $P_n = -17.16 \text{ dBm}$

³(c) $P_n = -15.35 \text{ dBm}$

⁴(d) $P_n = -30.67 \text{ dBm}$

Exercise 2 (1st, P4.3/2nd, P9.6)

The output noise of a circuit is measured to be -40 dBm around 100 kHz when a resolution bandwidth of 30 Hz is used. What is the expected dBm measurement if a resolution bandwidth of 10 Hz is used?⁵ Find the root spectral density in $\text{V}/\sqrt{\text{Hz}}$.^{6,7}

⁵ $V_{no-10\text{Hz}}^2 = -44.77 \text{ dBm}$

⁶ Spectral density $V_n^2(f) = 0.0033 \text{ (mV)}^2/\text{Hz}$

⁷ Root spectral density $V_n(f) = 0.058 \text{ mV}/\sqrt{\text{Hz}}$


Exercise 3 (1st, P4.4/2nd, P9.7)

At 0.1 Hz , a low frequency measurement has a noise value of -60 dBm when a resolution bandwidth of 1 mHz is used. Assuming $1/f$ noise dominates, what would be the expected noise value (in dBm) over the band from 1 mHz to 1 Hz ?⁸

⁸ $P_n = -31.6 \text{ dBm}$

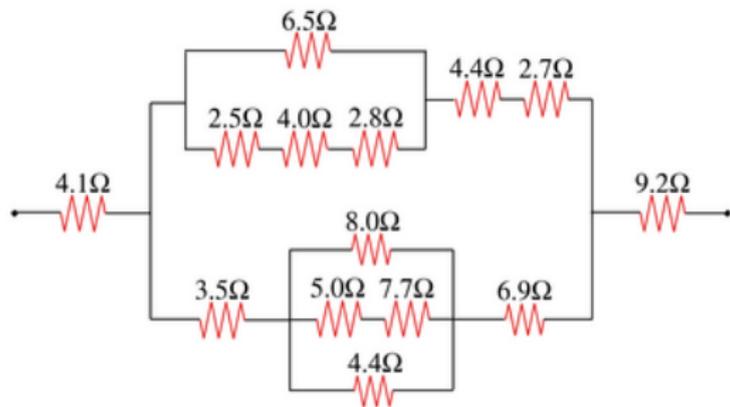Exercise 4 (1st, P4.5/2nd, P9.14)

Show that, when two resistors of values R_1 and R_2 are in series, their noise model is the same as a single resistance of value $R_1 + R_2$. Also compute the power spectral density across each resistance, as well as their serial combination. Repeat the problem for parallel resistances. What is the total power spectral density across the following resistance network?



Exercise 5 (1st/2nd, Example 9.5)

Consider a noise signal, $V_{ni}(f)$, that has a white root spectral density of $20 \text{ nV}/\sqrt{\text{Hz}}$. Find the total noise RMS value between DC and 100 kHz .⁹ What is the total noise RMS value if it is filtered by a RC filter with a cutoff frequency $f_0 = 1000 \text{ Hz}$, where it is assumed the RC filter is noise free?¹⁰

$$^9 V_{ni} = 6.3 \mu\text{V}$$

$$^{10} V_{no} = 0.79 \mu\text{V}$$


Exercise 6 (1st, P4.6/2nd, P9.15)

Sketch the spectral density of voltage noise across a 100 pF capacitor when it is in parallel with a $1 \text{ k}\Omega$ resistor. Make another sketch for the same capacitor but with a $1 \text{ M}\Omega$ resistance in parallel. What can you say about the area under the curves of the two sketches?¹¹

¹¹Whereas the curves are different, the area are the same: $V_{no}^2 = \frac{kT}{C}$

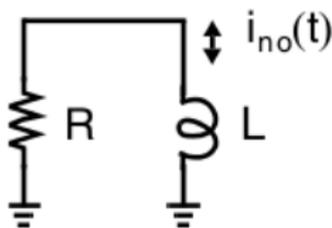Exercise 7 (1st, P4.9/2nd, P9.19)

Consider an inductor of value L and an arbitrary resistor in parallel, as shown in the following figure.



Show that the current noise is given by

$$I_{no}^2 = \frac{kT}{L}$$

Exercise 8 (2nd, Example 9.9)

Two voltage amplifiers (each having very large input impedance and small output impedance) are available: one with a gain of 3V/V and $3\mu\text{V}$ noise observed at the output; the other with a gain of 8V/V and $6\mu\text{V}$ noise observed at its output. What is the input-referred noise of each amplifier?¹² If the two amplifiers are to be placed in series to realize a gain of 24V/V , in what order should they be placed in order to obtain the best noise performance?¹³ What is the resulting input-referred noise of the overall system?¹⁴

¹² $V_{ni1} = 1\mu\text{V}$, $V_{ni2} = 0.75\mu\text{V}$

¹³ The second first

¹⁴ $V_{ni} = 0.76\mu\text{V}$