

Introduction to basics electronics principles

Bio-electronic, 2015

SCHMITZ Thomas

Department of Electrical Engineering and Computer Science,
University of Liège

February 25, 2015





- Basics principles
 - Components
 - Laws

- Common Mode

Section 1

Basics principles

Impedance

Ohms law :

$$U = R.I \quad (1)$$

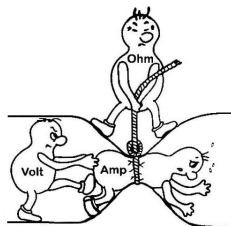


Figure: Ohms law

Impedance

Electrical impedance is the measure of the opposition that a circuit presents to a current when a voltage is applied.

It extends the concept of resistance to AC circuit.

$$Z(\omega) = \frac{U(\omega)}{I(\omega)} \quad (2)$$



Passive components

Component	Impedance	if frequency \nearrow impedance :
Resistor	R	\rightarrow
Capacitor	$\frac{1}{j\omega C}$	\searrow
Inductor	$j\omega L$	\nearrow



Kirchhoff law

nodes law

The sum of currents flowing into a node is equal to the sum of currents flowing out of that node

voltage law

The directed sum of the electrical potential differences (voltage) around any closed network is zero

usefull examples

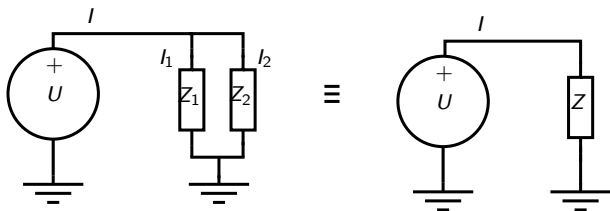


Figure: Parallel impedance

$$U = Z_1 \cdot I_1 = Z_2 \cdot I_2 = Z \cdot I$$

$$I_2 = \frac{Z_1}{Z_2} I_1 \quad (3)$$

$$I = I_1 + I_2$$

$$I = I_1 + \frac{Z_1}{Z_2} I_1 = I_1 \cdot \frac{Z_2 + Z_1}{Z_2} \quad (4)$$

$$Z \cdot I_1 \cdot \frac{Z_2 + Z_1}{Z_2} = Z_1 \cdot I_1$$

$$Z = \frac{Z_2 \cdot Z_1}{Z_1 + Z_2} \quad (5)$$

usefull examples

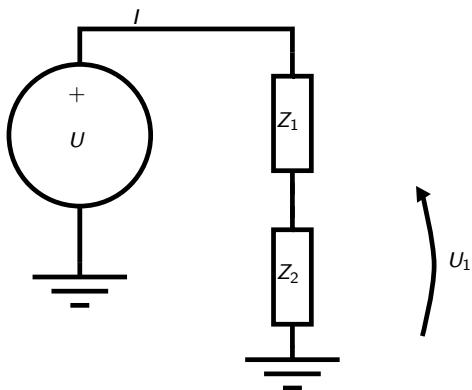


Figure: potentiometric divider


$$U = (Z_1 + Z_2) \cdot I$$
$$I = \frac{U}{Z_1 + Z_2} \quad (6)$$

$$U_1 = Z_2 \cdot I$$
$$U_1 = U \cdot \frac{Z_2}{Z_1 + Z_2} \quad (7)$$

Section 2

Common Mode

Common and differential mode voltage

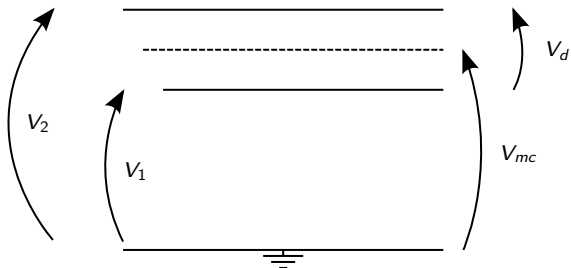


$$V_{mc} = \frac{V_1 + V_2}{2}$$


$$V_d = V_2 - V_1$$

Figure: Common mode voltage

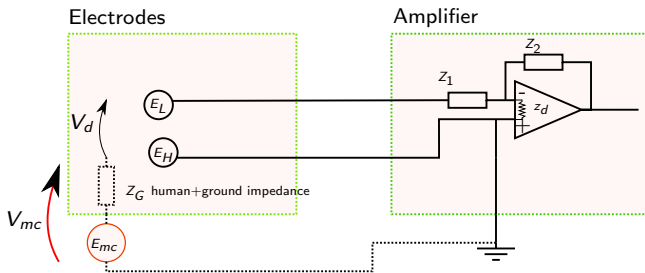Example : Electrodes to inverter amplifier



Common mode equivalent circuit

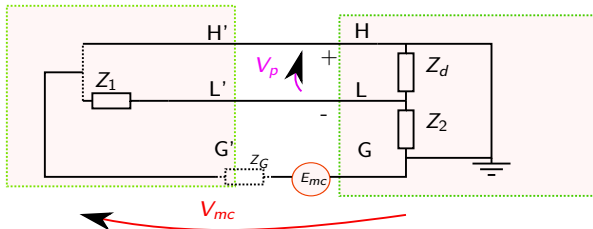

$$V_p = -\frac{Z_2}{Z_1 + Z_2} * V_{mc} = \text{no rejection of common mode parasites}$$