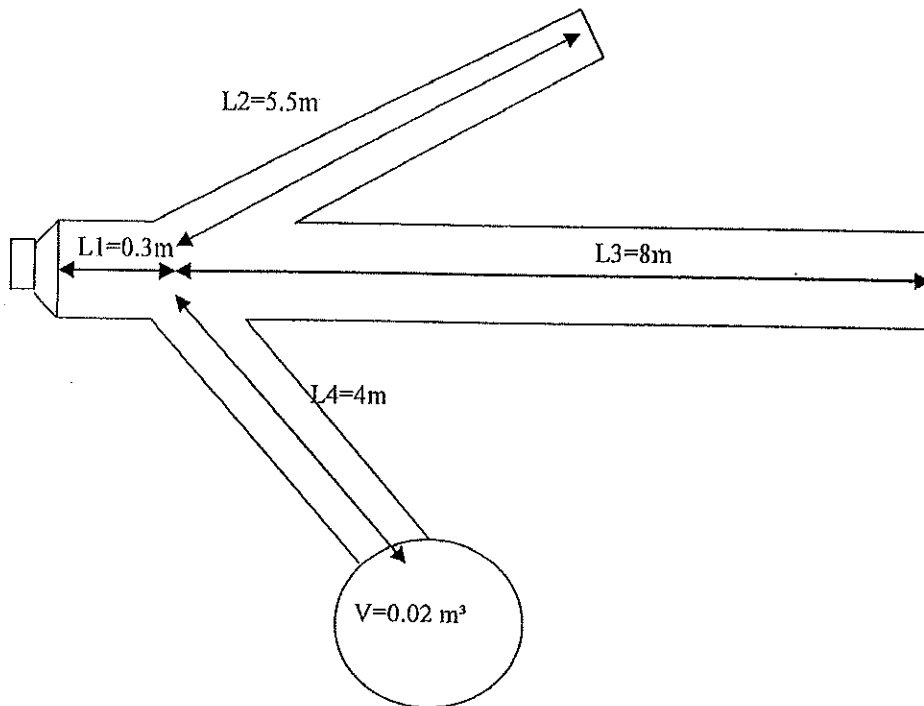


ELECTROACOUSTIC ANALOGIES – Exercise 1

The following acoustic system has an input pressure of P_{in} imposed by the loudspeaker in the figure. All the ducts have a circular section with a diameter of 20cm. The duct with length L_2 is closed by a rigid surface, the duct with the length L_3 ends with the opening of an infinite rigid baffle and the duct with length L_4 ends in a sphere of volume 0.02 m^3 .



Questions :

- 1) Draw the analog electric circuit of this system at the frequency 85 Hz.
- 2) What is the acoustic impedance presented to the loudspeaker (input impedance) at this frequency ?
- 3) Give the mathematical expression of the acoustic power radiated at this frequency.

Data :

The sphere can be modelled by an acoustic capacitance (lumped circuit element).

$$c = 340 \text{ m/s} \quad \rho_0 = 1.2 \text{ kg/m}^3$$

ELECTROACOUSTIC ANALOGIES – Exercise 2

The following acoustic system is driven by a loudspeaker emitting a sinusoidal signal (pure tone).

The volumes are the following:


$$\begin{array}{ll} V_1 = 2000 \text{ cm}^3 & \Phi_1 = 10 \text{ cm} \\ V_3 = 2000 \text{ cm}^3 & \Phi_2 = 3 \text{ cm} \end{array}$$

The cavities V_1 and V_3 can be modelled by lumped circuit elements and the effect of the connection between L_1 , L_2 and L_3 can be neglected.

Data: $c=344 \text{ m/s}$ and $\rho_0 = 1.2 \text{ kg/m}^3$.


Questions :

- 1) Draw the analog electric circuit of this system and mention the frequency limits for each element;
- 2) If the plane wave condition is valid for all the circuit elements, what is the minimum length of L_2 able to cancel any radiated power at 500 Hz ?
- 3) Is it possible to reach the same goal by replacing the duct L_2 by an Helmholtz resonator composed of a tube with $L_2=5\text{cm}$ and diameter $\Phi_2= 3 \text{ cm}$, connected with a volume V_2 (lumped circuit element) ? if so, calculate the value of V_2 ;
- 4) What is the input acoustic impedance at 1000 Hz in the original system (question 2) if the following conditions are established:
 $L_2=L_4=L_5$ and $L_1=L_3=L_2/2$?

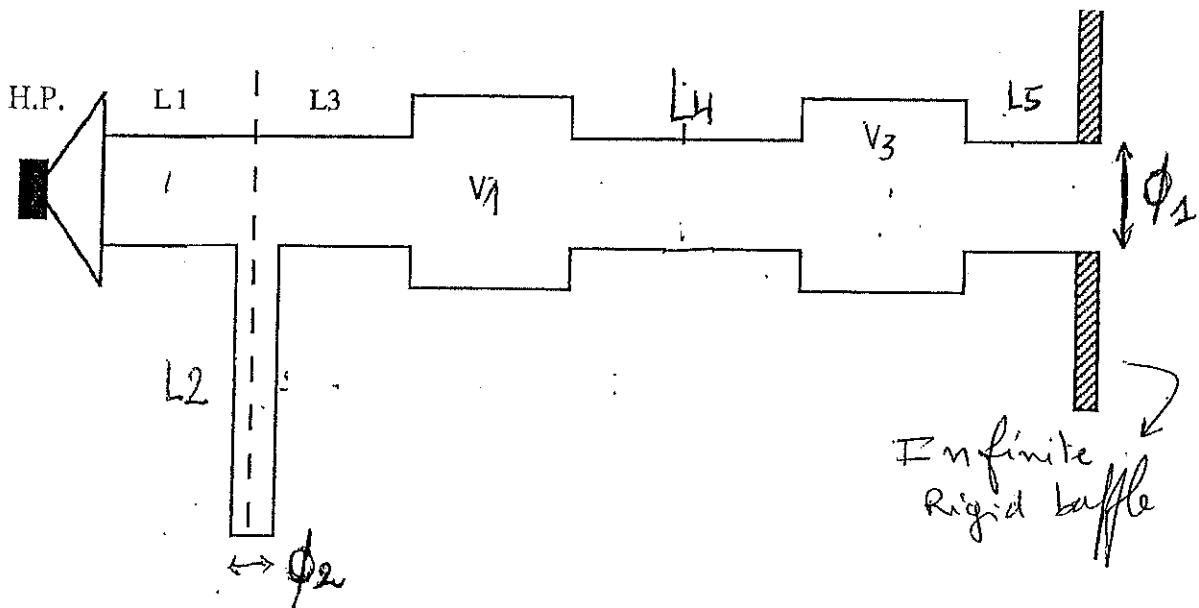

Exercise 5

Give the analog electrical circuit of the following acoustic system (the *artificial ear*):

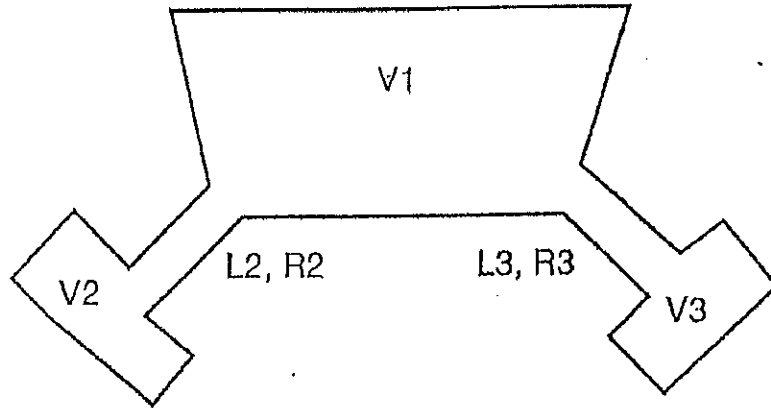


Exercise 6

The following acoustic system is composed of several tubes having the same diameter 5cm. Their length is a fraction of the same length " $l = 2.15\text{m}$ " ($1, 1/2$ or $1/4$). The two spheres are identical and have the same diameter of 10cm. The output of the system radiates in an infinite rigid baffle.

$C = 344 \text{ m/s}$.

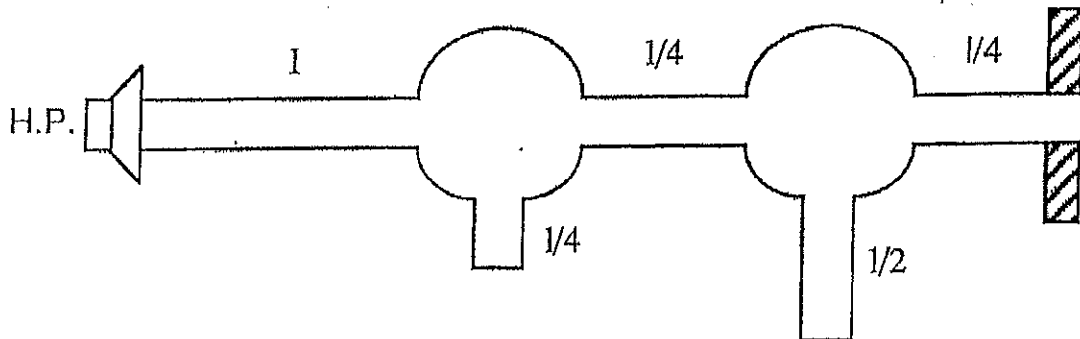Questions:

- Give the analog electrical circuit
- Compute the input acoustic impedance as seen by the loudspeaker (sound 'generator') at the entrance of the system. The emitted signal is a pure tone at 80 Hz.



Solution :

$$Z_{in} = -j 538000 \text{ (Pa} \cdot \text{s/m}^2\text{)} \quad \text{(capacitive)}$$