

Exercise: page 573 of the reference Book.

Find the capacitance values needed for a first-order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. It is also desired that the filter have zero gain at 50 kHz and the dc gain be unity. Assume $C_A = 10$ pF.

Exercise: page 573 of the reference Book.

Find the capacitance values needed for a first-order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. It is also desired that the filter have zero gain at 50 kHz and the dc gain be unity. Assume $C_A = 10$ pF.

Specification of Filter:

CT

Exercise: page 573 of the reference Book.

Find the capacitance values needed for a first-order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. It is also desired that the filter have zero gain at 50 kHz and the dc gain be unity. Assume $C_A = 10$ pF.

Specification of Filter:
CT

designer:
DT

Exercise: page 573 of the reference Book.

Find the capacitance values needed for a first-order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. It is also desired that the filter have zero gain at 50 kHz and the dc gain be unity. Assume $C_A = 10$ pF.

Specification of Filter:

CT

$h(s)$

Laplace domain

designer:


DT

$H(z)$

z -domain


s -domain

s -plane

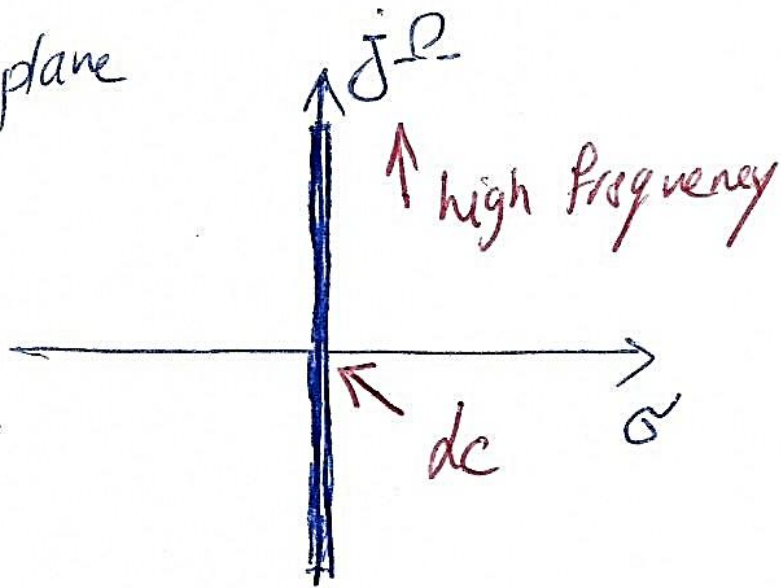


$$s = j\Omega$$


z -domain

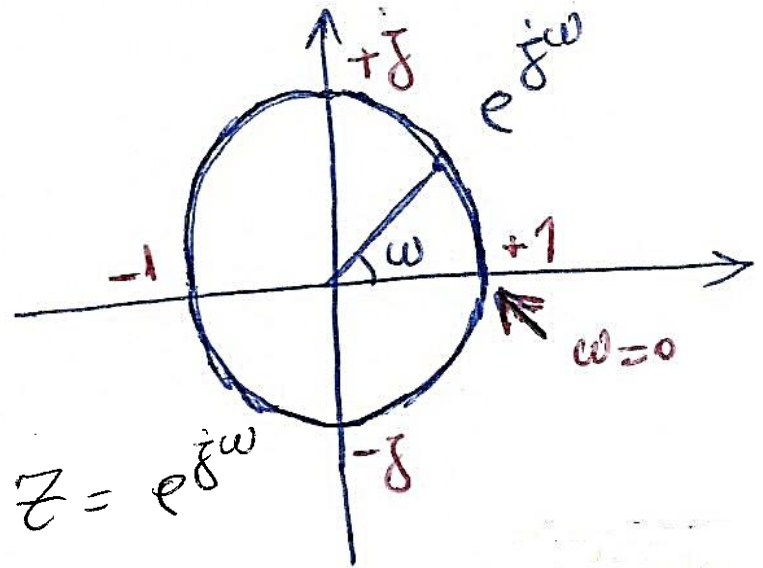

s -domain

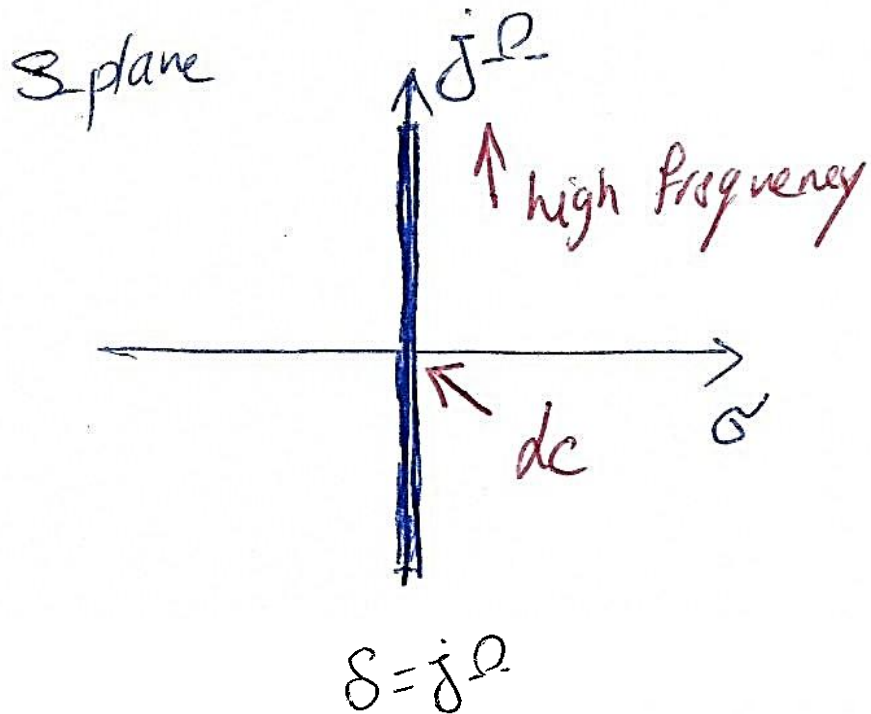


z -domain

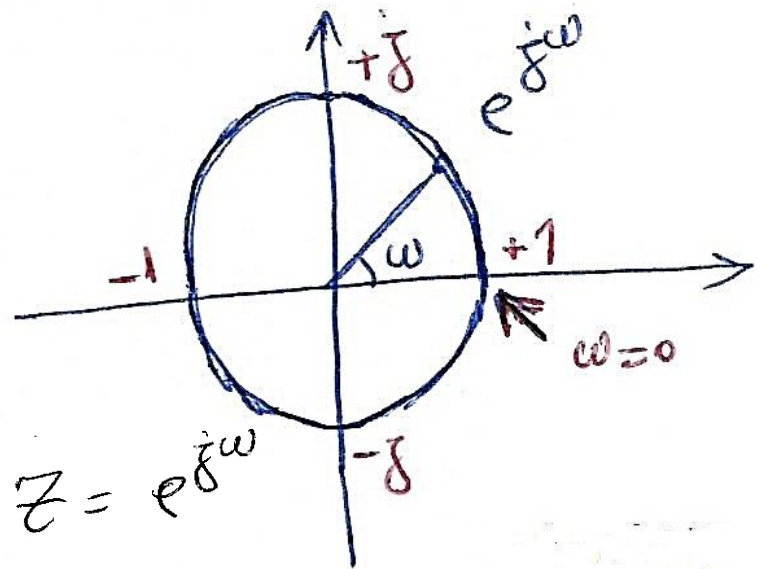

$$\Omega = \tan\left(\frac{\omega}{2}\right)$$


Bilinear Transform:

$$s = \frac{z-1}{z+1}$$

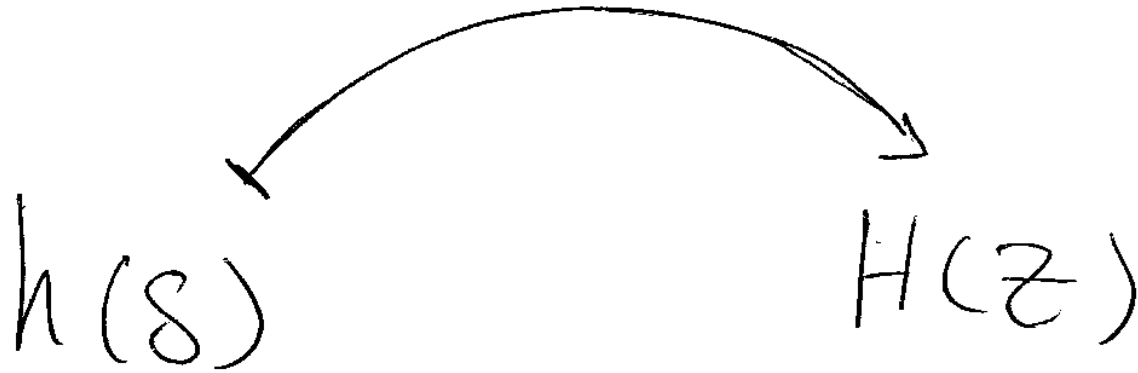

Bilinear Transform:

$$s = \frac{z-1}{z+1}$$

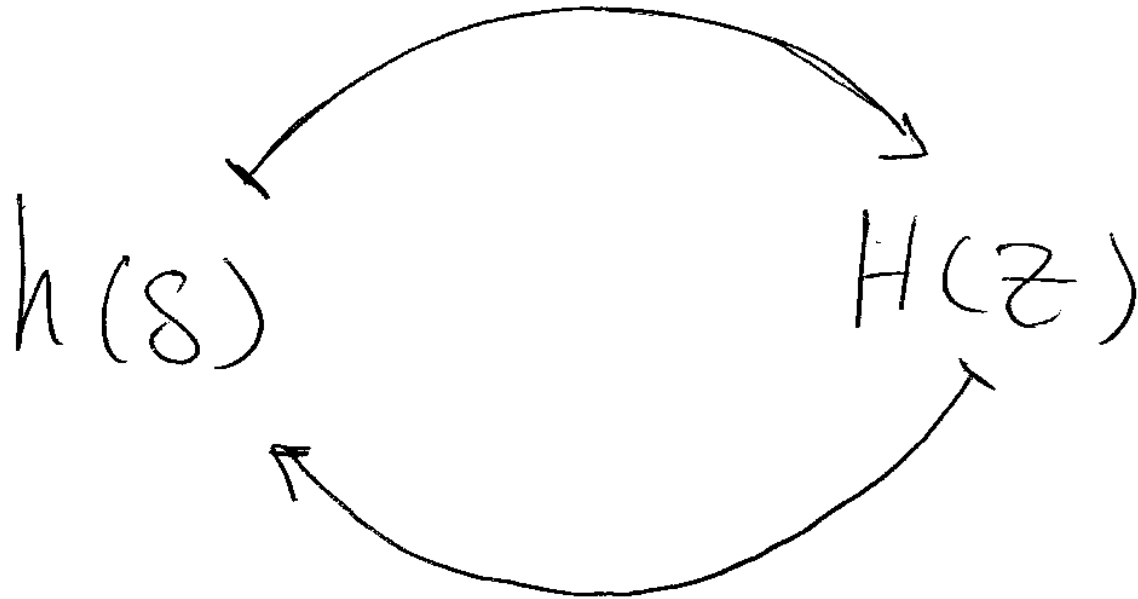

$$z = \frac{1+s}{1-s}$$

Page 550 of reference book (13.5.4, bilinear transform)

Golden relations

Golden relations

$$\left\{ \begin{array}{l} \omega = 2\pi f / f_s \quad ; \quad f_s: \text{clock freq} \\ \underline{\Omega} = \tan(\omega/2) \end{array} \right.$$

$$z = e^{j\omega}$$

Golden relations

For first order filters,

$$\delta_p = -\Omega_{3dB}$$

Golden relations

For first order filters,

$$\delta_p = -\Omega_{3dB}$$

$$z_p = \frac{1 + \delta_p}{1 - \delta_p}$$

Golden relations

For first order filters,

$$\delta_p = -\Omega_{3dB}$$

$$z_p = \frac{1 + \delta_p}{1 - \delta_p}$$

Crazy But true!

Exercise: page 573 of the reference Book.

Find the capacitance values needed for a first-order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. It is also desired that the filter have zero gain at 50 kHz and the dc gain be unity. Assume $C_A = 10$ pF.

$$f_{3-dB} = 10 \text{ kHz}$$

$$f_s = 100 \text{ kHz}$$

zero @ 50 kHz

$$H(1) = 1$$

$$C_A = 10 \text{ pF}$$

Exercise: page 573 of the reference Book.

$$\begin{cases} z = e^{j\omega} \\ \omega = \frac{f}{f_s} \cdot 2\pi \end{cases}$$

Exercise: page 573 of the reference Book.

$$\begin{cases} z = e^{j\omega} \\ \omega = \frac{f}{f_s} \cdot 2\pi \end{cases} \Rightarrow z_{\text{zero}} = e^{j \cdot 2\pi \cdot \frac{50}{100}} = e^{j\pi}$$

Exercise: page 573 of the reference Book.

$$\begin{cases} z = e^{j\omega} \\ \omega = \frac{f}{f_s} \cdot 2\pi \end{cases} \Rightarrow z_{\text{zero}} = e^{j \cdot 2\pi \cdot \frac{50}{100}} = e^{j\pi} =$$

Exercise: page 573 of the reference Book.

$$\begin{cases} z = e^{j\omega} \\ \omega = \frac{f}{f_s} \cdot 2\pi \end{cases} \Rightarrow z_{\text{zero}} = e^{j \cdot 2\pi \cdot \frac{50}{100}} = e^{j\pi} = -1$$

Exercise: page 573 of the reference Book.

$$\begin{cases} z = e^{j\omega} \\ \omega = \frac{f}{f_s} \cdot 2\pi \end{cases} \Rightarrow z_{\text{zero}} = e^{j \cdot 2\pi \cdot \frac{50}{100}} = e^{j\pi} = -1$$

$$\Rightarrow \boxed{z_{\text{zero}} = -1}$$

Exercise: page 573 of the reference Book.

$$\omega_{3-dB} = 2\pi \cdot \frac{f_{3-dB}}{f_s} = 2\pi \cdot \frac{10}{100} = 0.2\pi$$

Exercise: page 573 of the reference Book.

$$\omega_{3\text{-dB}} = 2\pi \cdot \frac{f_{3\text{-dB}}}{f_s} = 2\pi \cdot \frac{10}{100} = 0.2\pi$$

$$\Omega_{3\text{dB}} = \tan\left(\frac{\omega_{3\text{dB}}}{2}\right) = \tan\left(\frac{0.2\pi}{2}\right) = 0.3249$$

Exercise: page 573 of the reference Book.

$$\omega_{3\text{-dB}} = 2\pi \cdot \frac{f_{3\text{-dB}}}{f_s} = 2\pi \cdot \frac{10}{100} = 0.2\pi$$

$$\Omega_{3\text{dB}} = \tan\left(\frac{\omega_{3\text{dB}}}{2}\right) = \tan\left(\frac{0.2\pi}{2}\right) = 0.3249$$

$$\delta_p = -\Omega_{3\text{dB}} \Rightarrow \delta_p = -0.3249$$

Exercise: page 573 of the reference Book.

$$\omega_{3\text{-dB}} = 2\pi \cdot \frac{f_{3\text{-dB}}}{f_s} = 2\pi \cdot \frac{10}{100} = 0.2\pi$$

$$\Omega_{3\text{dB}} = \tan\left(\frac{\omega_{3\text{dB}}}{2}\right) = \tan\left(\frac{0.2\pi}{2}\right) = 0.3249$$

$$\delta_p = -\Omega_{3\text{dB}} \Rightarrow \delta_p = -0.3249$$

$$z_p = \frac{1 + \delta_p}{1 - \delta_p} = 0.5095$$

Exercise: page 573 of the reference Book.

$$H(z) = \frac{k(z+1)}{z - 0.5095}$$

Exercise: page 573 of the reference Book.

$$H(z) = \frac{k(z+1)}{z - 0.5095}$$

From $H(1) = 1 \longrightarrow k = 0.24525$

Exercise: page 573 of the reference Book.

$$H(z) = \frac{k(z+1)}{z - 0.5095}$$

From $H(1) = 1 \longrightarrow k = 0.24525$

$$H(z) = \frac{0.24525(z+1)}{z - 0.5095}$$

Exercise: page 573 of the reference Book.

$$H(z) = \frac{k(z+1)}{z - 0.5095}$$

From $H(1) = 1 \rightarrow k = 0.24525$

$$H(z) = \frac{0.24525(z+1)}{z - 0.5095}$$

or equivalently,

$$H(z) = \frac{0.4814z + 0.4814}{1.9627z - 1}$$

Exercise: page 573 of the reference Book.

From the Course

$$A(z) = \frac{\left(\frac{C_1 + C_2}{C_A}\right) z^{-C_1/C_2}}{\left(1 + \frac{C_3}{C_A}\right) z^{-1}}$$

Exercise: page 573 of the reference Book.

From the Course

$$A(z) = \frac{\left(\frac{C_1 + C_2}{C_A}\right)z - C_1/C_2}{\left(1 + \frac{C_3}{C_A}\right)z^{-1}}$$

$$C_1 = 4.814 \text{ PF}$$

$$C_2 = -9.628 \text{ PF}$$

$$C_3 = 9.628$$

Exercise: page 573 of the reference Book.

From the Course

$$A(z) = \frac{\left(\frac{C_1 + C_2}{C_A}\right)z - C_1/C_2}{\left(1 + \frac{C_3}{C_A}\right)z^{-1}}$$

$$C_1 = 4.814 \text{ pF}$$

$$C_2 = -9.628 \text{ pF} \rightarrow \text{(differential input can realize the negative capacitance)}$$

$$C_3 = 9.628$$

page 573

Exercise 1

First order Filter

$$H(z) = \frac{-\left(\frac{c_1 + c_2}{C_A}\right)z + c_3/C_A}{\left(1 + \frac{c_3}{C_A}\right)z - 1} = \frac{kz + A}{z - z_p}$$

$$f_{3-dB} = 10 \text{ kHz}$$

$$f_s = 100 \text{ kHz}$$

zero @ $z = 0$

Exercise 1

First order Filter

$$H(z) = \frac{-\left(\frac{c_1 + c_2}{C_A}\right)z + c_3/C_A}{\left(1 + \frac{c_3}{C_A}\right)z - 1} = \frac{kz + A}{z - z_p}$$

$$f_{3-dB} = 10 \text{ kHz}$$

$$f_s = 100 \text{ kHz}$$

$$\text{zero @ } z=0 \Rightarrow A=0$$

Exercise 1

First order Filter

$$H(z) = \frac{-\left(\frac{c_1 + c_2}{C_A}\right)z + c_3/C_A}{\left(1 + \frac{c_3}{C_A}\right)z - 1} = \frac{kz + A}{z - z_p}$$

$$f_{3-dB} = 10 \text{ kHz}$$

$$f_s = 100 \text{ kHz}$$

$$\text{zero @ } z=0 \Rightarrow A=0$$

$$H(1) = 1$$

Exercise 1

First order Filter

$$H(z) = \frac{-\left(\frac{c_1 + c_2}{C_A}\right)z + c_3/C_A}{\left(1 + \frac{c_3}{C_A}\right)z - 1} = \frac{kz + A}{z - z_p}$$

$$f_{3-dB} = 10 \text{ kHz}$$

$$f_s = 100 \text{ kHz}$$

$$\text{zero @ } z=0 \Rightarrow A=0$$

$$H(1) = 1 \Rightarrow \frac{k}{1 - z_p} = 1 \Rightarrow k = 1 - z_p$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s}$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s} = 2\pi \times \frac{10}{100} = 0.2\pi$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s} = 2\pi \times \frac{10}{100} = 0.2\pi$$

$$\Omega_{3-dB} = \tan\left(\frac{\omega_{3-dB}}{2}\right)$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s} = 2\pi \times \frac{10}{100} = 0.2\pi$$

$$\Omega_{3-dB} = \tan\left(\frac{\omega_{3-dB}}{2}\right) = \tan(0.2\pi) = 0.3049 \frac{\text{rad}}{\text{sample}}$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s} = 2\pi \times \frac{10}{100} = 0.2\pi$$

$$\Omega_{3-dB} = \tan\left(\frac{\omega_{3-dB}}{2}\right) = \tan(0.2\pi) = 0.3049 \frac{\text{rad}}{\text{sample}}$$

$$\delta_p = -\Omega_{3-dB} = -0.3049$$

Exercise 1

$$\omega_{3-dB} = 2\pi \times \frac{f_{3-dB}}{f_s} = 2\pi \times \frac{10}{100} = 0.2\pi$$

$$\Omega_{3-dB} = \tan\left(\frac{\omega_{3-dB}}{2}\right) = \tan(0.2\pi) = 0.3044 \frac{\text{rad}}{\text{sample}}$$

$$s_p = -\Omega_{3-dB} = -0.3044$$

$$z_p = \frac{1+s_p}{1-s_p} = 0.53327$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

$$\left\{ \begin{array}{l} A=0 \rightarrow C_1 = 0 \text{ PF} \\ C_A = 10 \text{ PF} \end{array} \right.$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

$$\left\{ \begin{array}{l} A=0 \rightarrow C_1 = 0 \text{ PF} \\ C_A = 10 \text{ PF} \end{array} \right.$$

$$z_p = \frac{C_A}{C_A + C_3}$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

$$\left\{ \begin{array}{l} A=0 \rightarrow C_1 = 0 \text{ PF} \\ C_A = 10 \text{ PF} \end{array} \right.$$

$$z_p = \frac{C_A}{C_A + C_3} \Rightarrow C_3 = \frac{C_A(1 - z_p)}{z_p} = 8.752 \text{ PF}$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

$$\left\{ \begin{array}{l} A=0 \rightarrow C_1 = 0 \text{ PF} \\ C_A = 10 \text{ PF} \end{array} \right.$$

$$z_p = \frac{C_A}{C_A + C_3} \Rightarrow C_3 = \frac{C_A(1 - z_p)}{z_p} = 8.752 \text{ PF}$$

$$k = 1 - z_p$$

Exercise 1

$$H(z) = \frac{0.46673}{1 - 0.53327z^{-1}}$$

$$\left\{ \begin{array}{l} A=0 \rightarrow C_1 = 0 \text{ PF} \\ C_A = 10 \text{ PF} \end{array} \right.$$

$$z_p = \frac{C_A}{C_A + C_3} \Rightarrow C_3 = \frac{C_A(1 - z_p)}{z_p} = 8.752 \text{ PF}$$

$$k = 1 - z_p = \frac{-C_2/C_A}{1 + C_3/C_A} = \frac{-C_2}{C_A + C_3}$$

$$\Rightarrow C_2 = -k(C_A + C_3) = -8.752 \text{ PF}$$

Exercise 1

gain @ $f = 50 \text{ kHz}$

Exercise 1

gain @ $f = 50 \text{ kHz}$

$$\Rightarrow Z = e^{j\omega} = e^{j 2\pi f / f_s} = e^{j\pi} = -1$$

Exercise 1

gain @ $f = 50 \text{ kHz}$

$$\Rightarrow Z = e^{j\omega} = e^{j 2\pi f / f_s} = e^{j\pi} = -1$$

$$\Rightarrow H(-1) = \frac{0.46673}{1 + 0.53327} = 0.309$$

Exercise 1

gain @ $f = 50 \text{ kHz}$


$$\Rightarrow Z = e^{j\omega} = e^{j 2\pi f / f_s} = e^{j\pi} = -1$$

$$\Rightarrow H(-1) = \frac{0.46673}{1 + 0.53327} = 0.309 \xrightarrow{\text{20log}(\cdot)} -40.33 \text{ dB}$$


Exercise 2: How to draw Signal Flow graph

Circuit :

Non-switched Capacitor

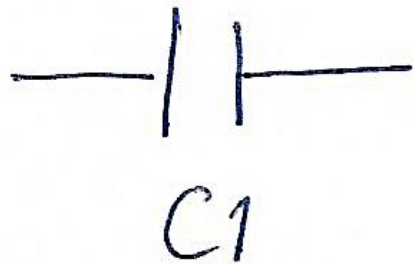

Flow Graph:

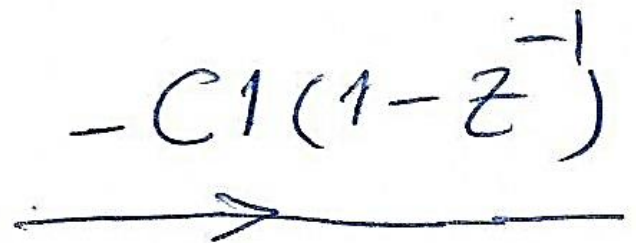


Exercise 2: How to draw Signal Flow graph

Circuit :

Flow Graph:


Non-delaying Switched Capa

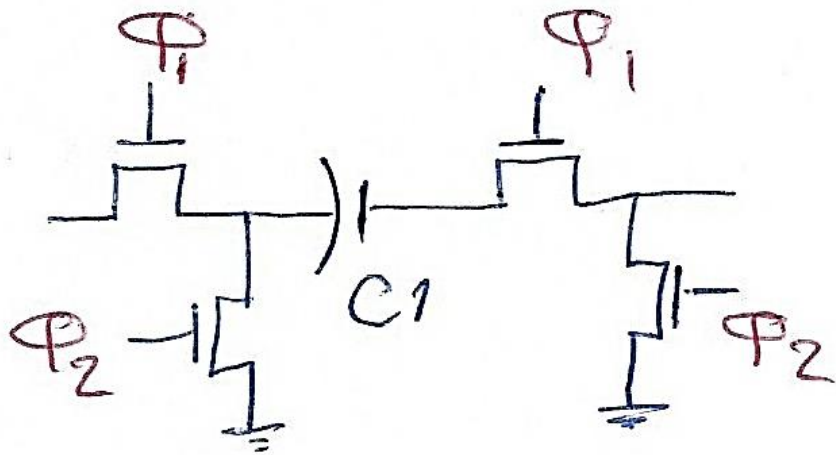


Exercise 2: How to draw Signal Flow graph

Circuit :

delaying Switched Capca

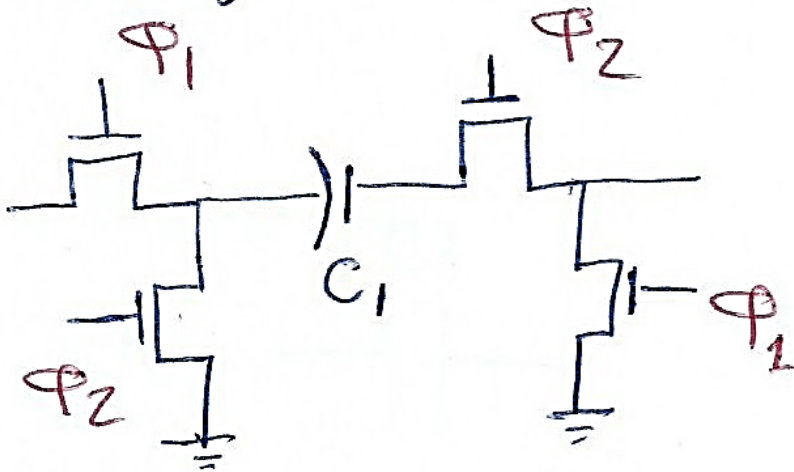


Flow Graph:

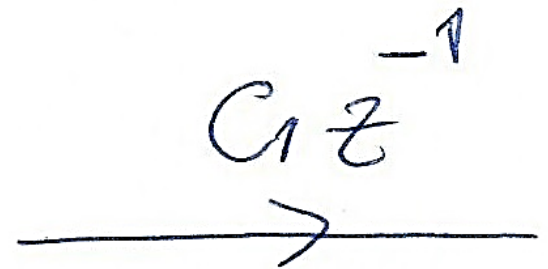



Exercise 2: How to draw Signal Flow graph



Circuit :


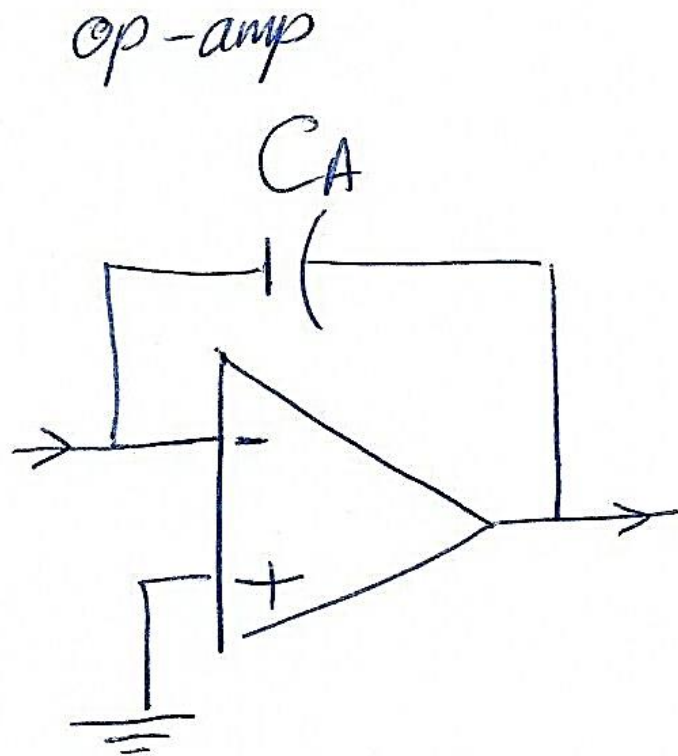




Flow Graph:

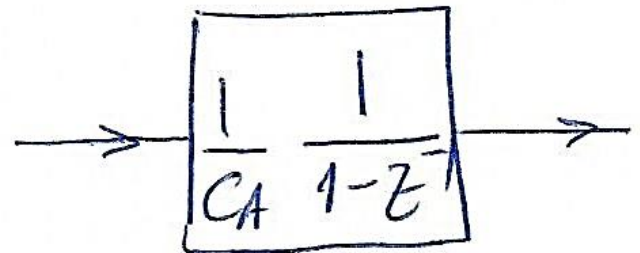

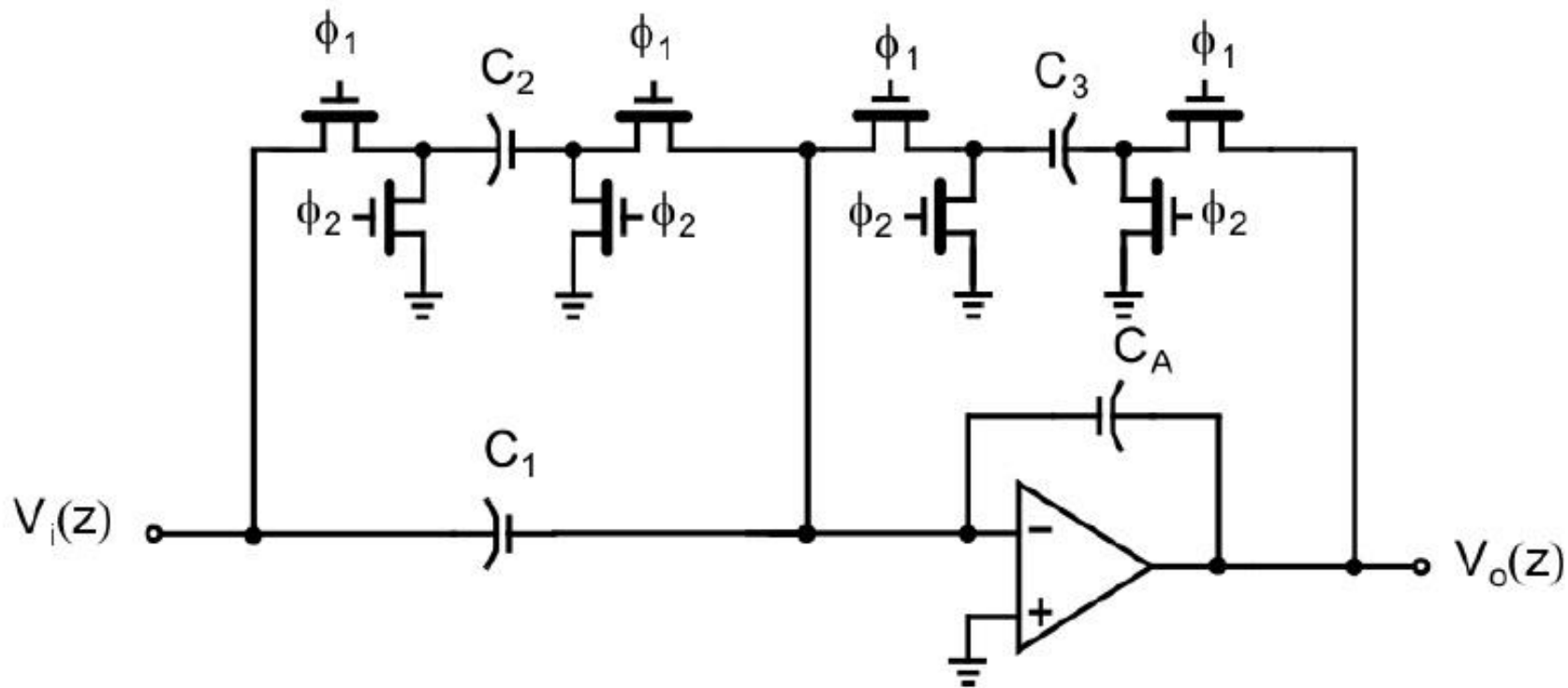


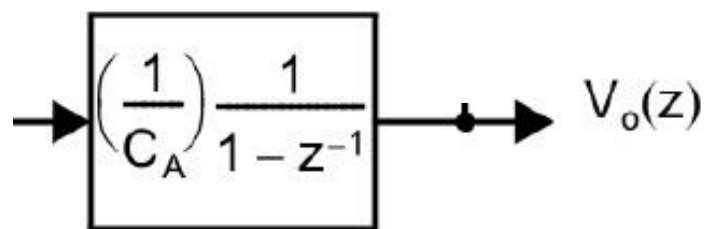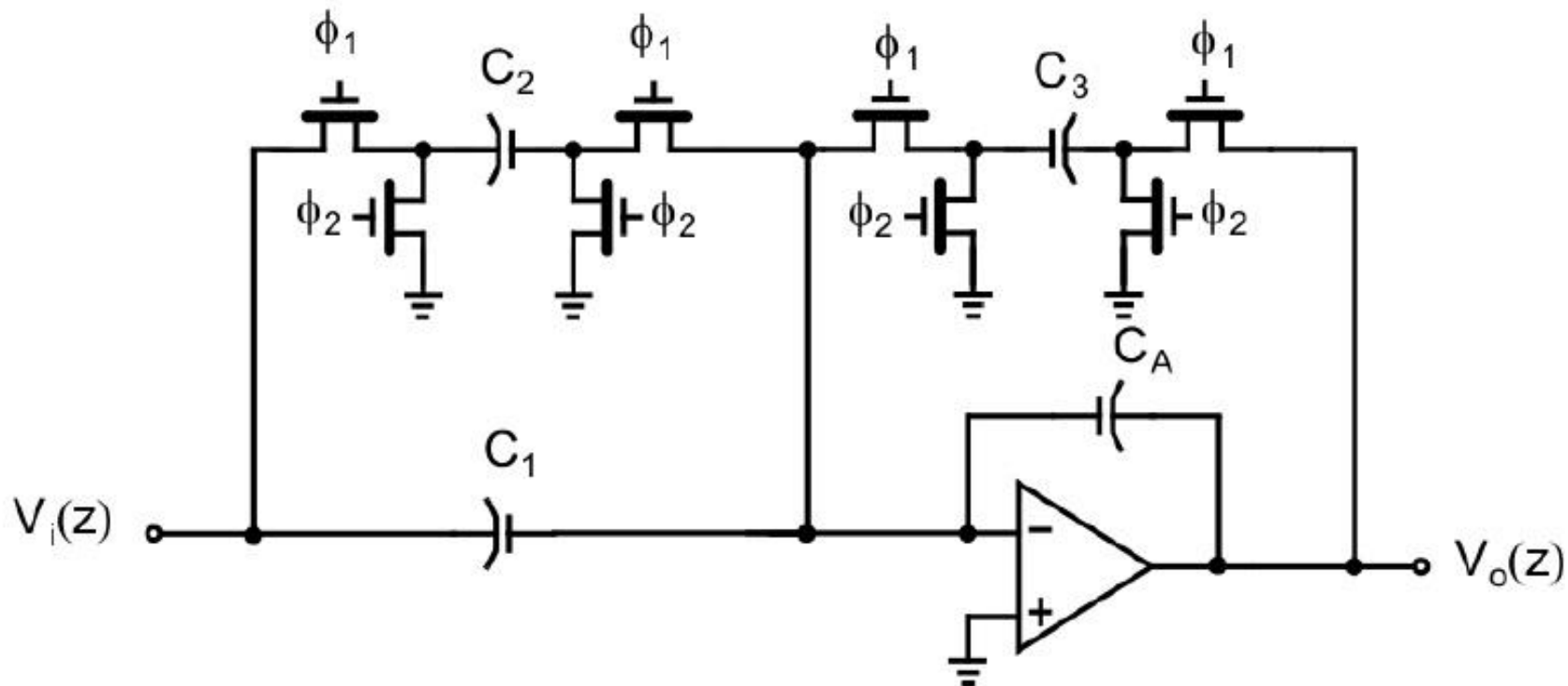

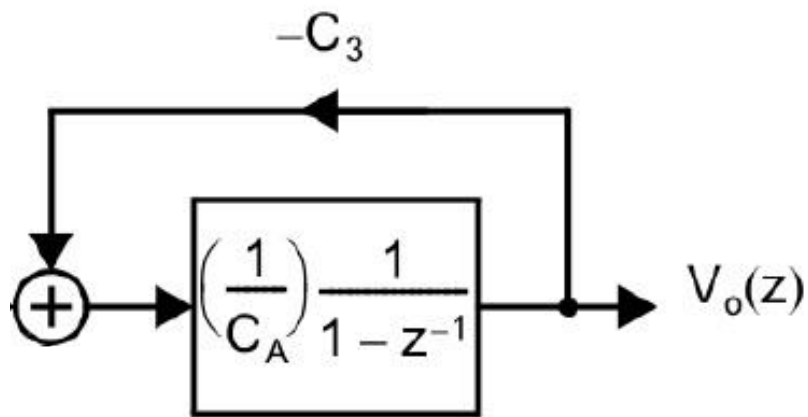
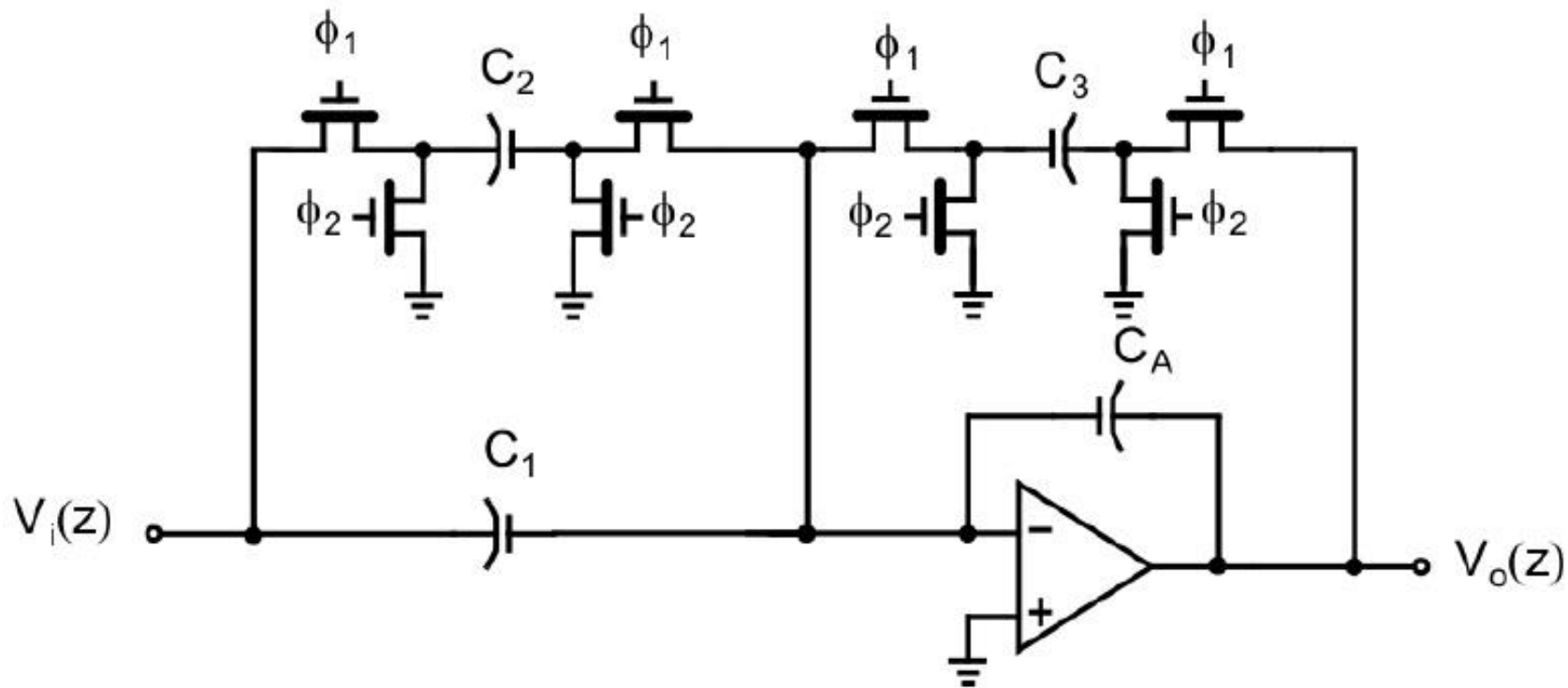


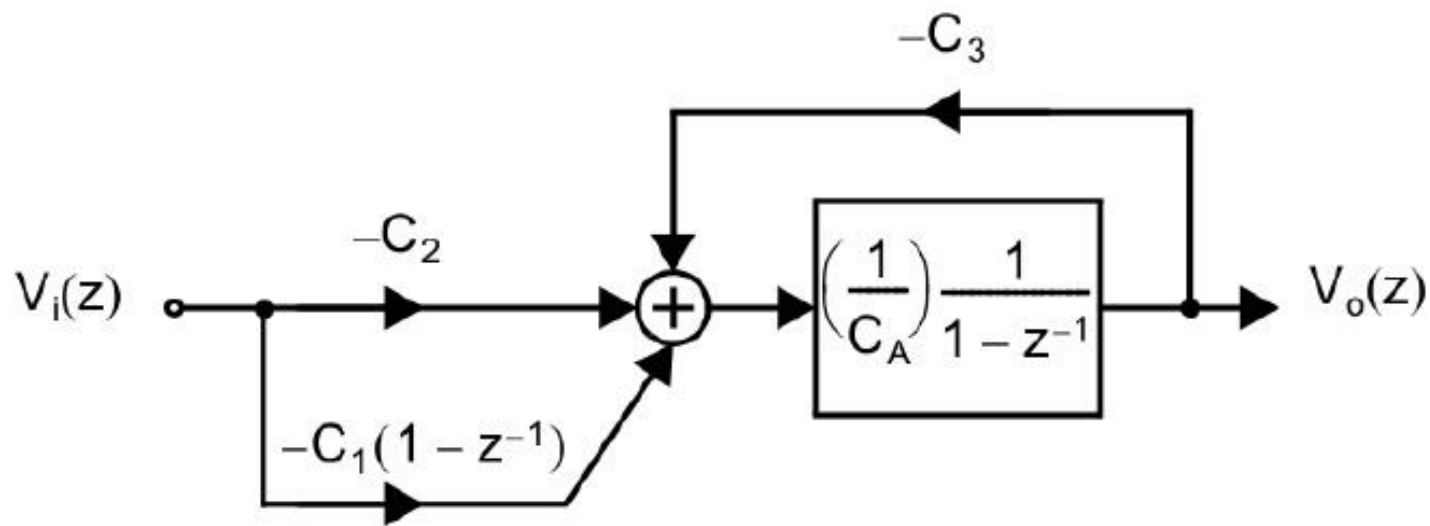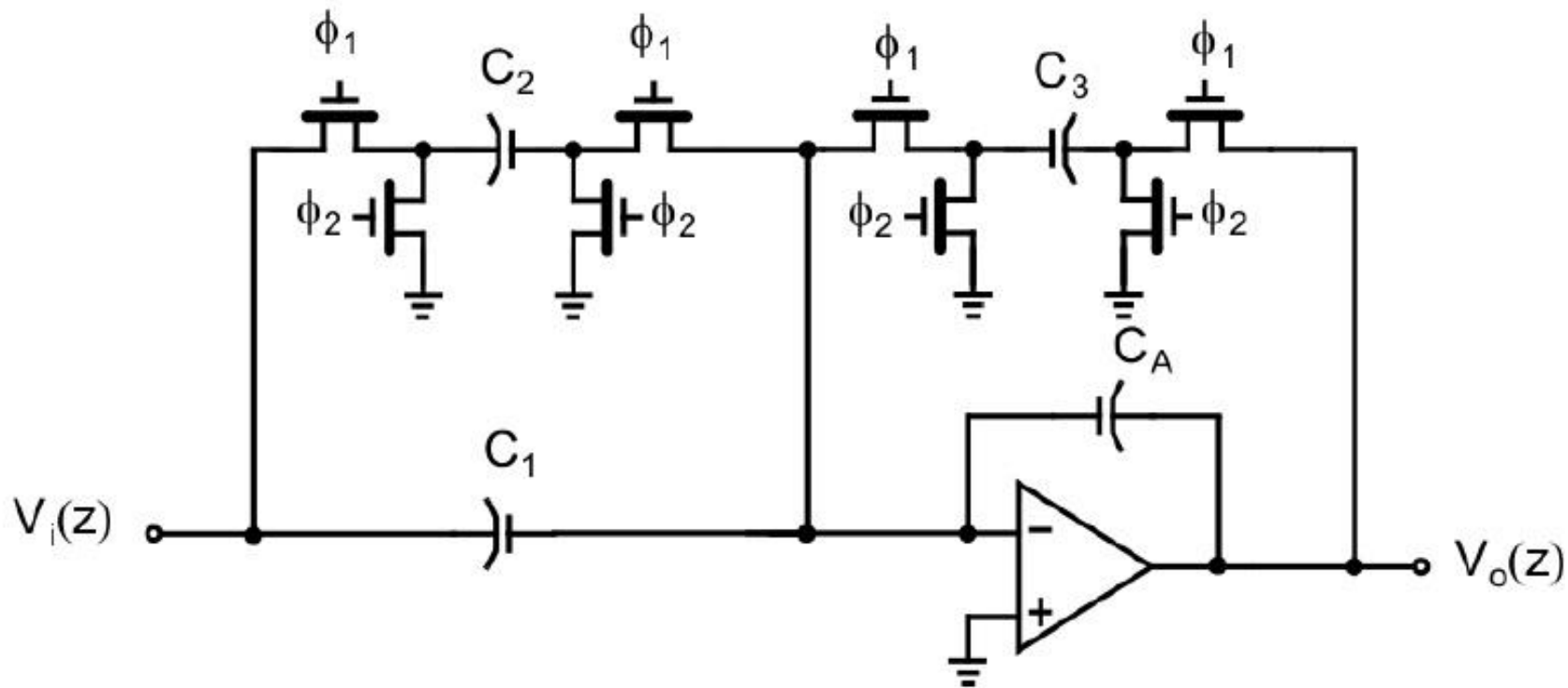



Exercise 5

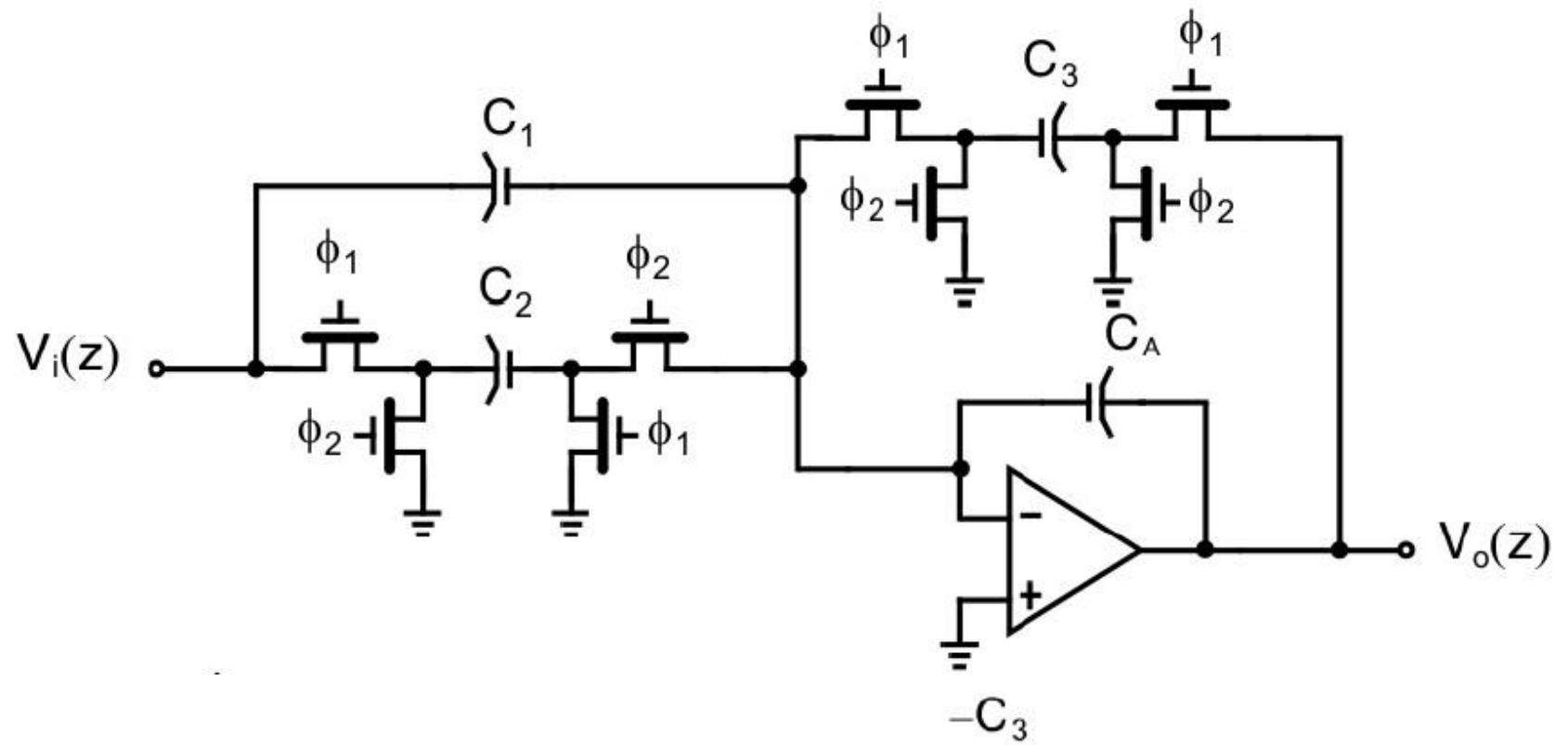


Exercise 5

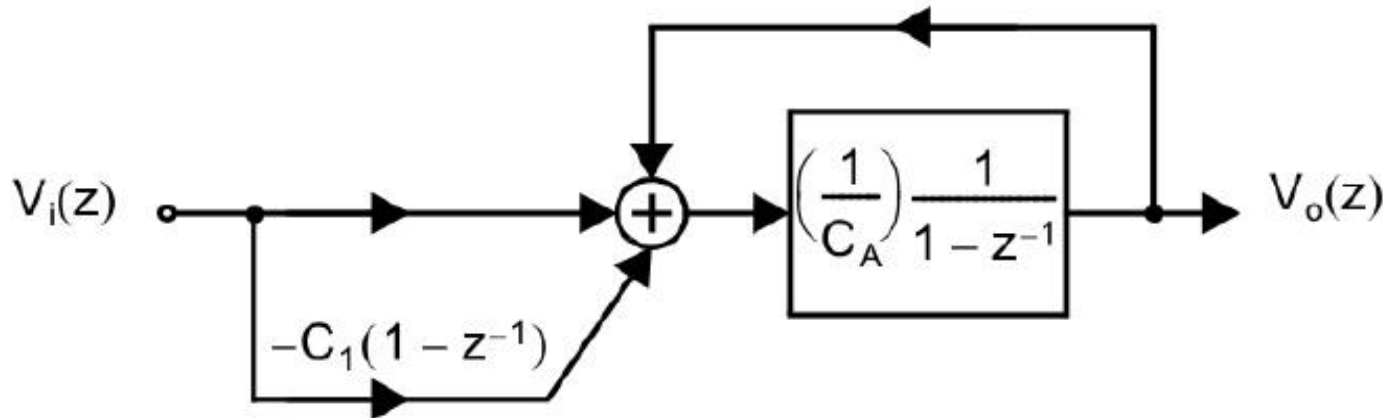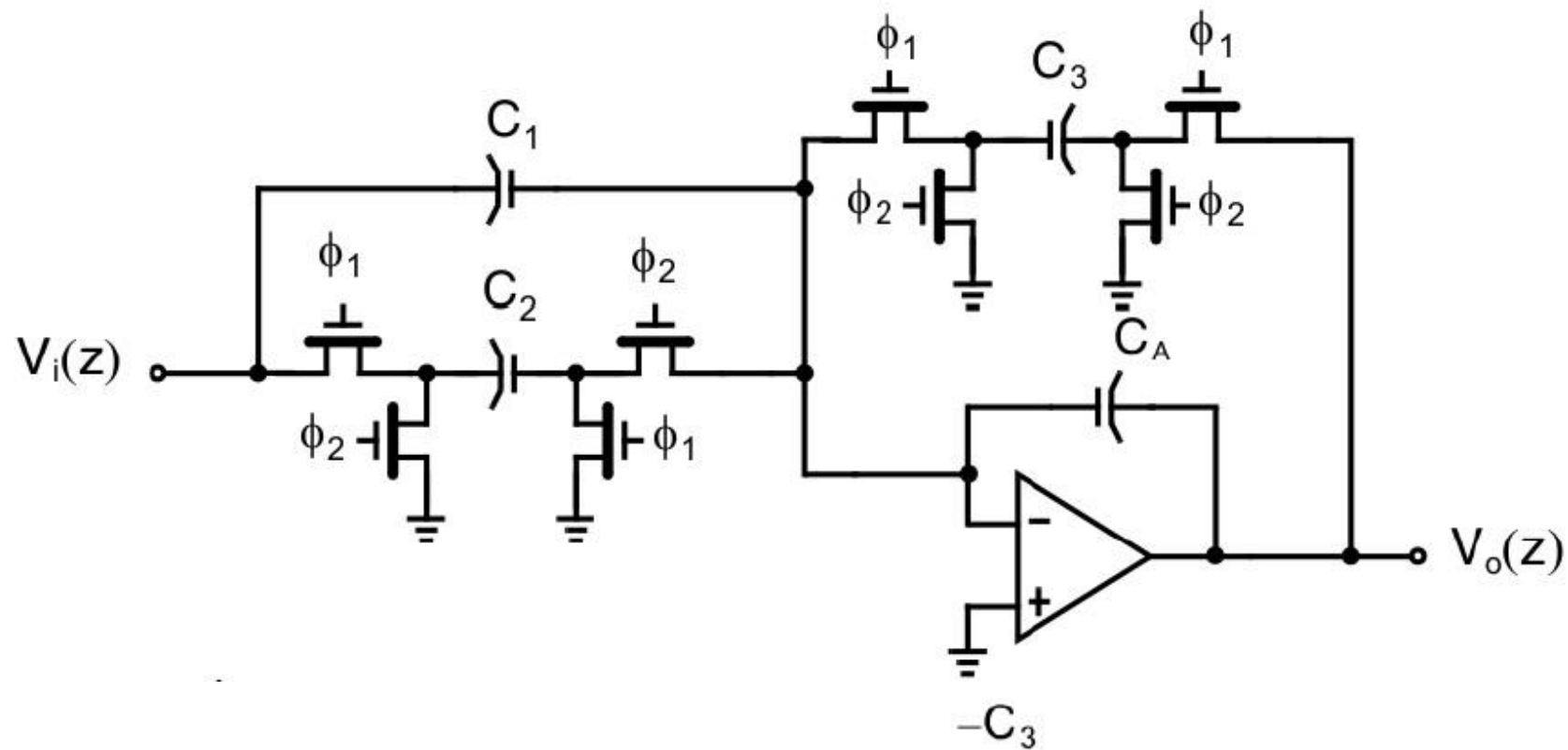


Exercise 5

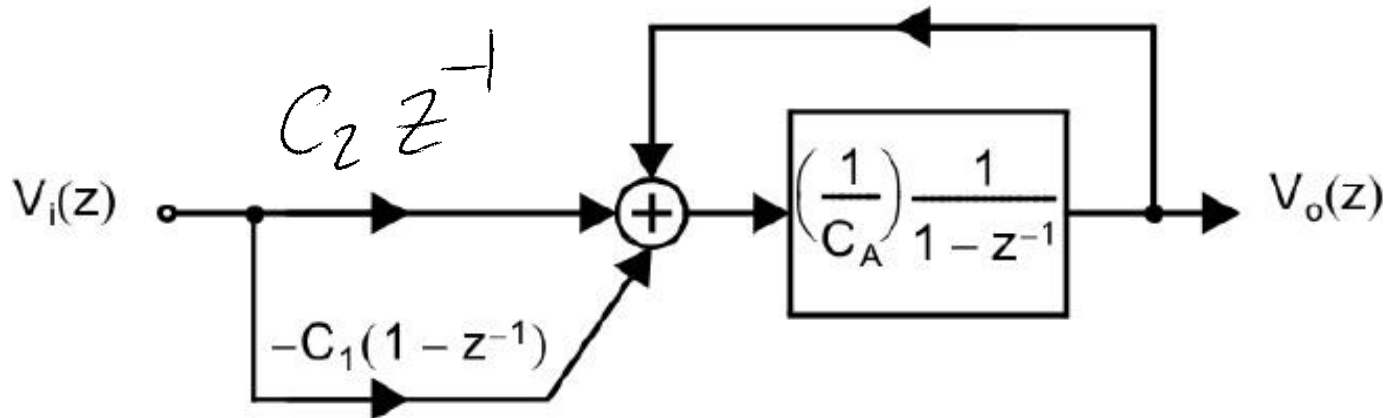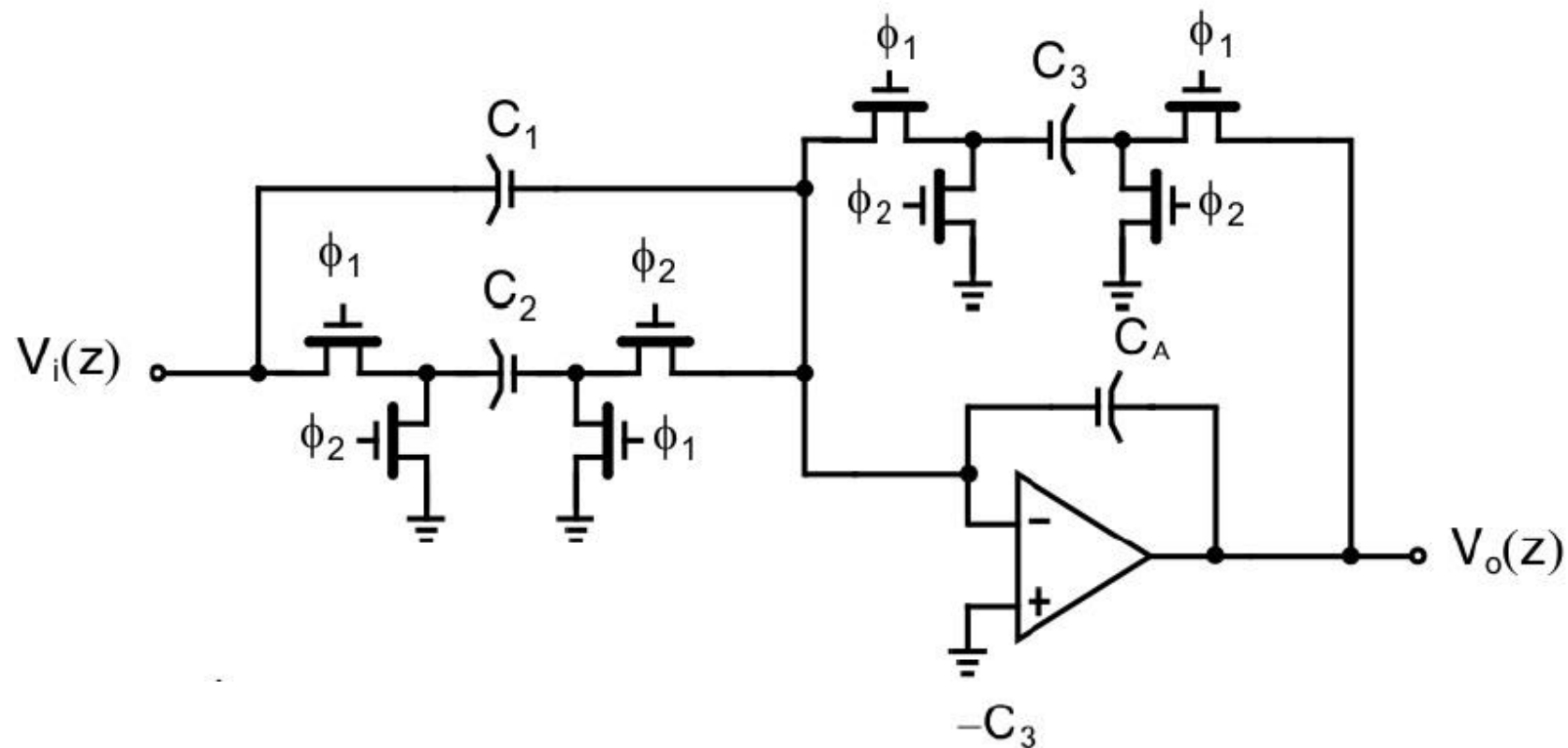

Exercise

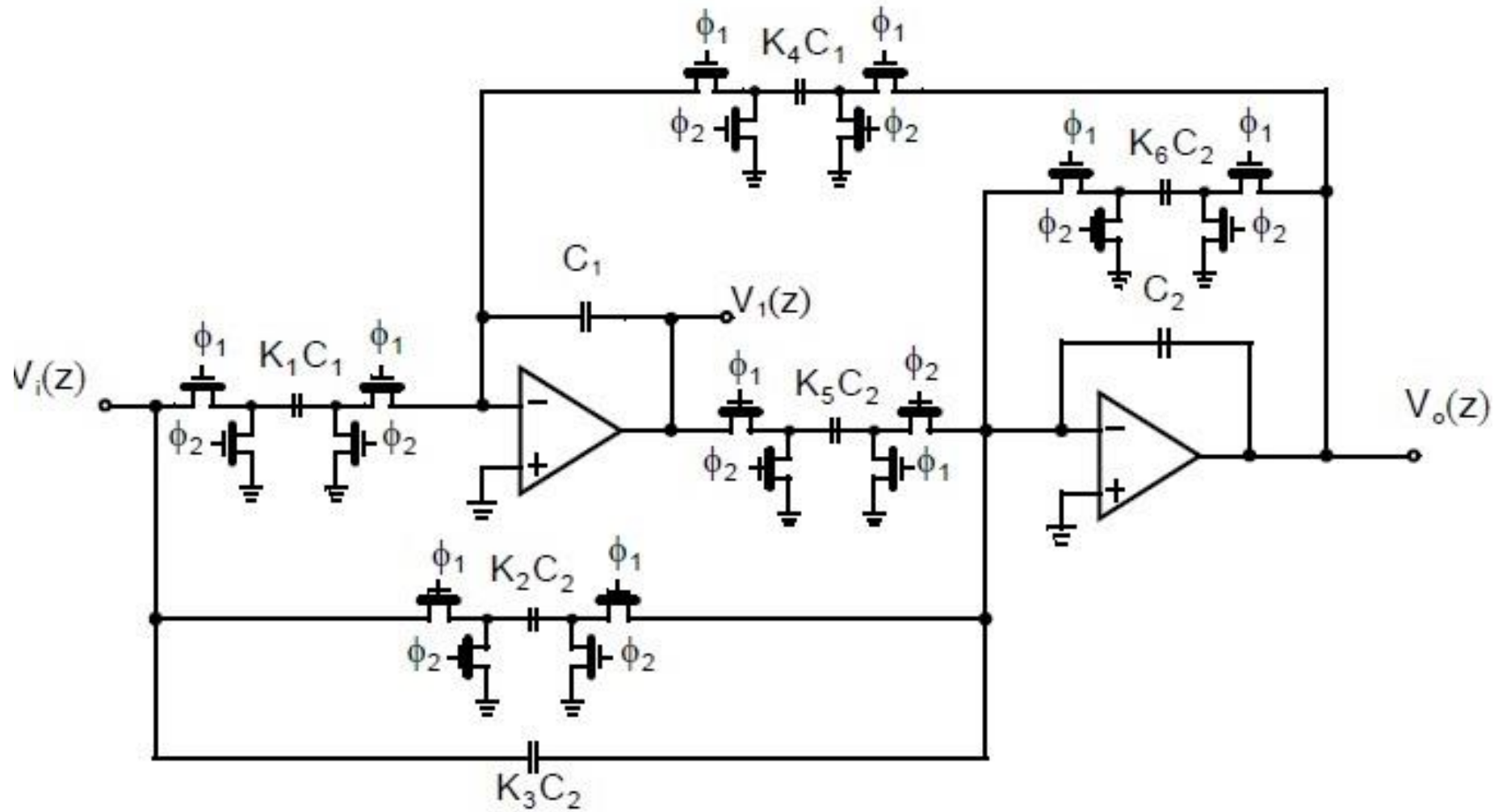

Exercise

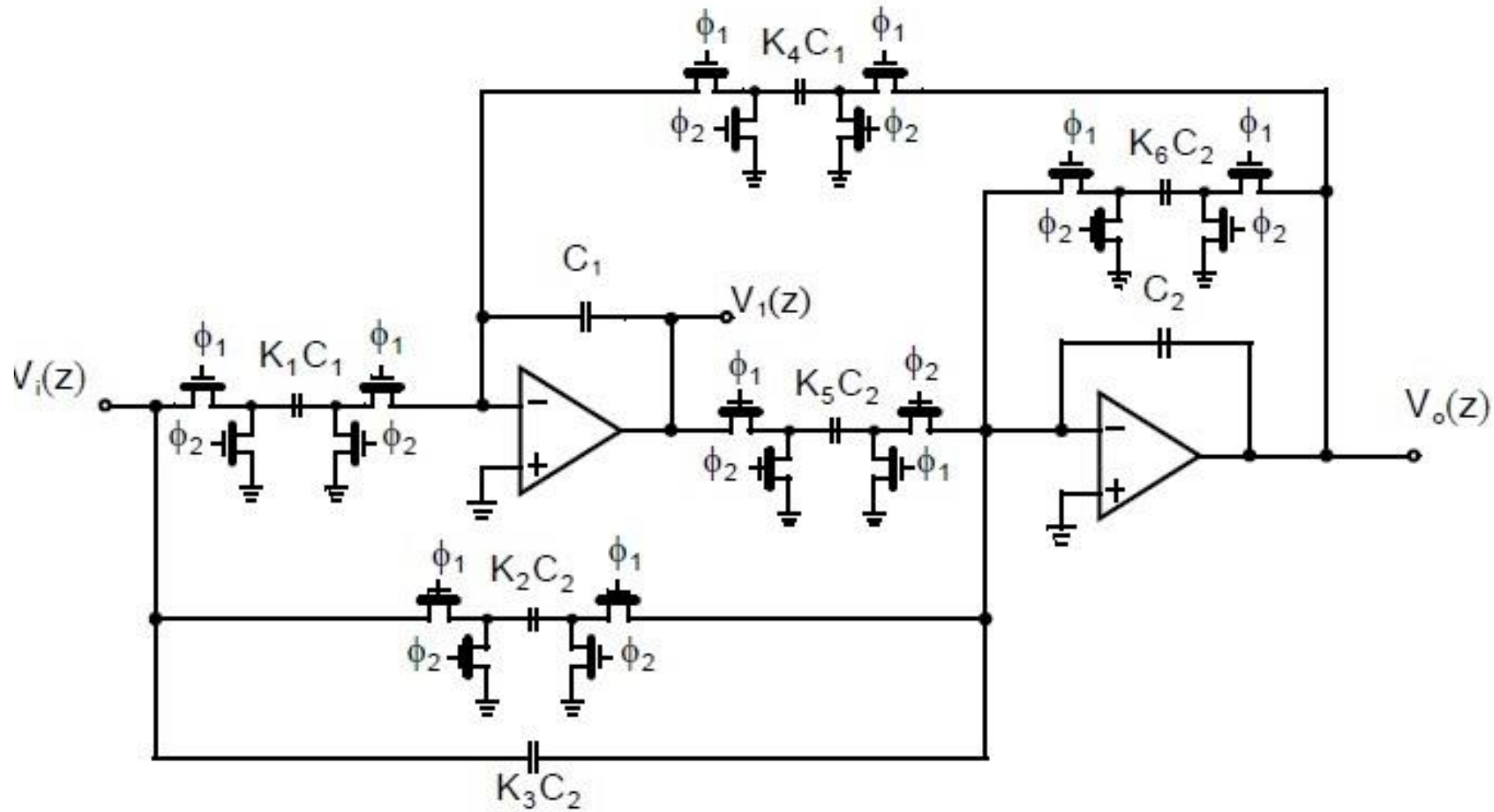

Exercise

